

EXPERIMENT: Kirchoff's Rules

**Objective:** To verify Kirchoff's rules:

**Loop Rule:** The sum of all potential differences encountered while going around any closed loop in a circuit is zero:  $\sum_i V_i = 0$ .


**N.B.** When going from (-) to the (+) terminal of an *emf* there is a positive difference of potential and when going through a resistor along the current direction there is a negative difference of potential. In the difference of potential ( $V_2 - V_1$ ),  $V_1$  is the previous and is the last value  $V_2$  first following a selected direction of circulation in circuit.

**Junction Rule:** The sum of all currents flowing into or out a junction in a circuit is zero:  $\sum_i I_i = 0$ .

**N.B.** A current flowing into the junction is considered positive while the current flowing out of a circuit is considered negative.

**Materials:** Three resistors  $R_1 = 20 \text{ Ohm}$ ,  $R_2 = 30 \text{ Ohm}$ ,  $R_3 = 100 \text{ Ohm}$ ; two 6V sources, a voltmeter and an ammeter.

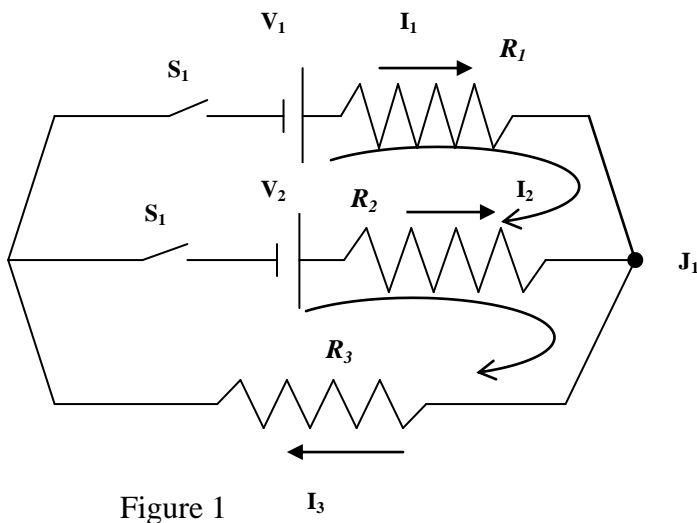**Procedures:** Before building the electric schemas, measure and record the precise resistance values by using a multimeter.



- Connect the circuit shown in figure 1
- Switch the switches  $S_1, S_2$ .
- **Measure** and record “quickly” the terminal voltage  $V_1, V_2$  of two sources using the voltmeter, and three current values  $I_1, I_2$  and  $I_3$  using the ammeter.
- As far as finished with these measurements, switch off  $S_1, S_2$  to avoid the discharge of batteries.
- Use the measured values  $V_1, V_2, I_1, I_2$  and  $I_3$  in formulas ( 1,2,3 ) and verify if they transform them to identities . Use the uncertainty calculations to prove this.

Figure 1


After selecting the circulation direction as shown in the figure the Kirchoff's rules give:

**Loop \_1:**  $V_1 - I_1 * R_1 + I_2 * R_2 - V_2 = 0 \rightarrow R_1 * I_1 - R_2 * I_2 = V_1 - V_2$  (1)

**Loop \_2:**  $V_2 - I_2 * R_2 - I_3 * R_3 = 0 \rightarrow R_2 * I_2 + R_3 * I_3 = V_2$  (2)

**Junction \_J1:**  $I_1 + I_2 - I_3 = 0 \rightarrow I_1 + I_2 = I_3$  (3)

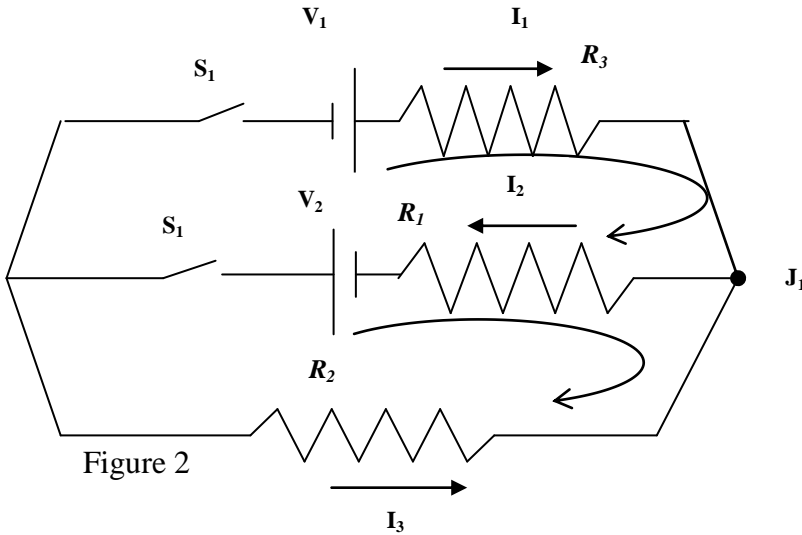Next, build the scheme presented in figure 2 by inverting the poles of battery 2. Write three equations ( $1'$ ,  $2'$ ,  $3'$ ) derived from the Kirchoff's rules for the scheme in figure 2. Measure and record  $V_1, V_2, I_1, I_2$  and  $I_3$ . Repeat the procedure of verifications the same way you did for the scheme in figure 1.



### Calculations

- Put the measured values for terminal voltages  $V_1, V_2$ , and resistors' values  $R_1, R_2, R_3$ , in the equation ( $1', 2', 3'$ ) derived from Kirchoff's rules for the scheme in figure 2.
- Calculate the three current values  $I_{1t}, I_{2t}$  and  $I_{3t}$  from these equations.
- Compare the calculated values with the measured values  $I_1, I_2$  and  $I_3$ .

### **Conclusions:**

- 1- Do your measured data satisfy the Kirchoff's rules at junction  $J_1$  and around the two loops for the scheme in figure 1?
- 2- Do your theoretical calculations based on Kirchoff's rules fit with measured values for currents corresponding to the scheme in figure 2?