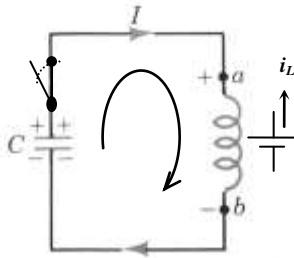


## 12.1 OSCILLATION OF ELECTRIC VARIABLES IN A LC CIRCUIT

- Let's consider a circuit that contains only a capacitor  $C$  and an ideal inductor  $L$  in series (see fig.1). Assume that at  $t = 0$  the capacitor has a charge " $Q_0$ ". At this moment one turns the switch "on" and the charge of capacitor  $C$  starts flowing in circuit by building a current " $I$ " directed as shown in the figure. The increase of flux into the inductor gives rise to an induced  $\varepsilon_L$  (and related  $i_L$ ) with the "opposite" polarity as shown in figure. The second rule of Kirchhoff (start from "-" plate of capacitor) gives

$$V_C(t) - \varepsilon_L = \frac{Q(t)}{C} - L \frac{dI(t)}{dt} = 0 \quad (1)$$



As  $\frac{dQ}{dt} < 0$  and  $I > 0$ , the current  $I$  is equal to "-" change rate of

charge  $Q$  in capacitor plates. So, one gets  $I(t) = -\frac{dQ(t)}{dt}$  (\*)

Then, by substituting relation (\*) in eq.1 one gets

Fig.1

$$\frac{Q(t)}{C} + L \frac{d^2}{dt^2} Q(t) = 0 \rightarrow \frac{d^2}{dt^2} Q(t) + \frac{1}{LC} Q(t) = 0 \quad (2)$$

By noting  $\omega_0^2 = \frac{1}{LC}$  -i.e.-  $\omega_0 = \sqrt{\frac{1}{LC}}$ , the eq.(2) takes the form  $\frac{d^2}{dt^2} Q(t) + \omega_0^2 Q(t) = 0$  (3)

This is the equation of SHO and its solution has the form  $Q(t) = Q_0 \sin(\omega_0 t + \varphi)$  (4)

At  $t = 0$ ,  $Q = Q_0$  that fixes  $\varphi = \pi/2$ . So,  $Q(t) = Q_0 \sin(\omega_0 t + \pi/2) = Q_0 \cos(\omega_0 t)$  (5)

Then  $I(t) = -\frac{dQ(t)}{dt} = Q_0 \omega_0 \sin \omega_0 t = I_0 \sin \omega_0 t$  i.e. with  $I_0 = Q_0 \omega_0$   $I(t) = I_0 \sin \omega_0 t$  (6)

So, it comes out that: **if there is some energy stored in a LC circuit,**

**the circuit will generate a SHO with circular frequency  $\omega_0 = \sqrt{\frac{1}{LC}}$**

for the **current**, the **voltage** and the **charge in capacitor**.

Fig. 2 shows the variations of  $Q(t)$  and  $I(t)$  in time; the charge in capacitor and its voltage  $V_C = Q/C$  are **advanced** by  $\pi/2$  versus the current in circuit. When  $Q_C$  and  $V_C$  are maximum the **current in circuit is zero** (and vice versa). At  $t = 0$ , **all the energy** is electric and stocked **inside the capacitor** :

$$U_{E-max} = \frac{Q_0^2}{2C} \quad (7)$$

Fig.2

For  $t > 0$ , a part of the energy is stocked as **electric energy inside the capacitor**  $U_E = \frac{Q_0^2}{2C} \cos^2 \omega_0 t$  and

the other part as **magnetic energy inside the inductor**  $U_B = \frac{1}{2} L I_0^2 \sin^2 \omega_0 t$ ; so the **total energy in circuit**

$$\text{is } U = \frac{Q_0^2}{2C} \cos^2(\omega_0 t) + \frac{L I_0^2}{2} \sin^2(\omega_0 t) \quad (8)$$

Figure 3 presents the evolution of each part of of energy with time. Note that their sum is **all time constant** (like at any SHO) and when one of them is maximum the other one is zero.

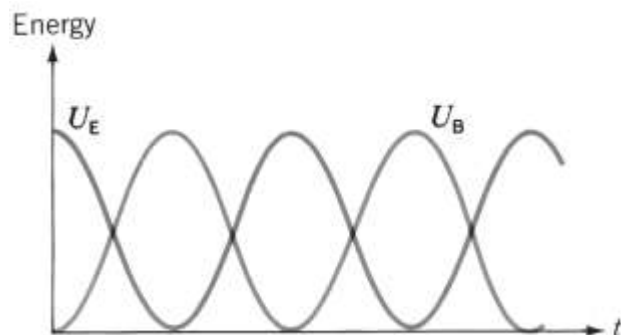


Fig 3

## 12.2 DAMPED OSCILLATIONS IN A CIRCUIT C, L, R

- In previous section we considered an *ideal inductor* with zero resistance and we got a result which is *ideal*; i.e. *SHO* for  $Q$ ,  $I$  and  $U$  in the circuit. This means oscillations that follow to infinite time. In the case of a real inductor, there is a resistance (*at least that of inductor*) in circuit and one deals with a circuit with C, L, R in series (fig.4). Assume that, at  $t = 0$ s, the capacitor has its maximum charge  $Q_0$ .

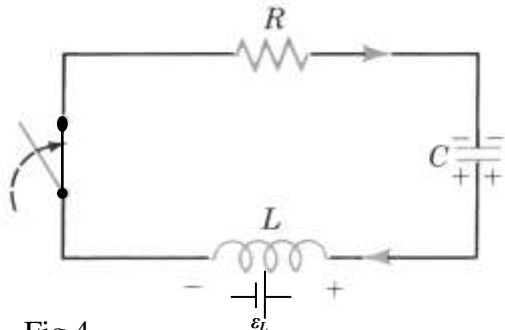


Fig.4

At this moment ( $t = 0$ ) one turns the circuit "on". By applying the second rule of Kirchhoff for a moment  $t > 0$ , one get

$$\frac{Q(t)}{C} - L \frac{dI}{dt} - IR = 0 \quad (9)$$

By using the expression (\*) for the current, one get

$$L \frac{d^2 Q(t)}{dt^2} + R \frac{dQ(t)}{dt} + \frac{Q(t)}{C} = 0 \quad (10)$$

This is the equation of a damped harmonic oscillation. One might remember the equation for damped

harmonic motions :  $m \frac{d^2 x(t)}{dt^2} + b \frac{dx(t)}{dt} + kx(t) = 0$  where  $b$  is the damping coefficient.

By referring to DHO (see oscillations in NYC folder), one finds out that the solution of (10) has the form

$$Q(t) = Q_0 * e^{-\left(\frac{R}{2L}\right)t} \sin(\omega' t + \varphi) \quad (11)$$

where the *damped circular frequency* is

$$\omega' = \sqrt{\omega_0^2 - \left(\frac{R}{2L}\right)^2} \quad (12)$$

The *un-damped circular frequency* for a C, L, R circuit corresponds to  $R = 0$  and is  $\omega_0 = \frac{1}{\sqrt{LC}}$  (13)

- The evolution of electric parameters ( $Q$ ,  $I$ ,  $U$ ) in circuit depends on the relative values of  $R$ ,  $L$  and  $C$ .

a) There is a *under damped* oscillation if  $R < 2\omega_0 L$ . The *amplitude* of oscillations for ( $Q$ ,  $I$ ,  $U$ ) *decays exponentially*. Example (Fig.5a):  $Q(t) = Q_0 * e^{-t/\tau}$  where  $\tau = 2L/R$  (14)

b) There are *critically damped* oscillations if  $R = 2\omega_0 L$ . Actually, in this case there are no oscillations in circuit. All electric variables just fall to zero the fastest way (Fig.5b-downside).

c) There are *over damped* oscillations if  $R > 2\omega_0 L$ . Even in this case there are no oscillations in circuit. All electric variables just fall to zero with time, but slowly (Fig.5b-graph upside).


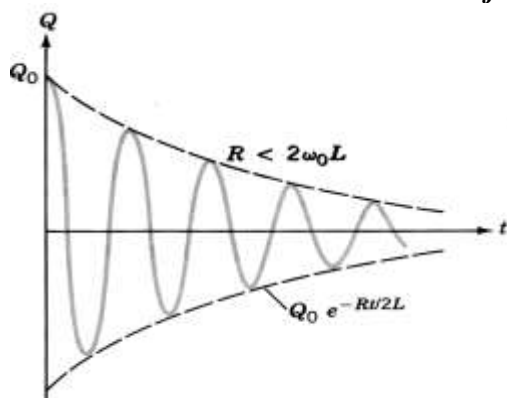


Fig.5

(a)

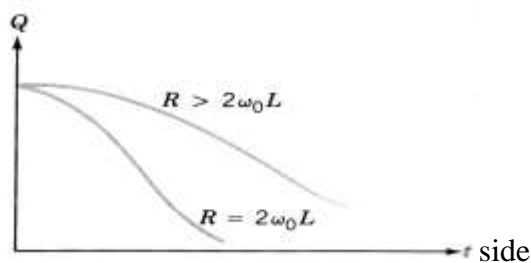

(b)