

12.1 OSCILLATION OF ELECTRIC VARIABLES IN A LC CIRCUIT

- Let's consider a circuit with a capacitor C and an inductor L in series (see fig.1); the capacitor has a charge "Q₀" at t = 0. At this moment one turns the switch on and the charge of capacitor C starts flowing into the circuit; it will build a current "I" as shown in fig. The increase of flux into the inductor gives rise to an induced ε_L (and related i_L) with the polarity shown in figure. The second rule of Kirchoff (start from "-" plate of capacitor) gives

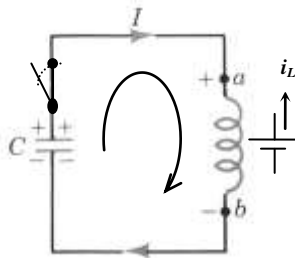


Fig.1

$$V_C(t) - \varepsilon_L = \frac{Q(t)}{C} - L \frac{dI(t)}{dt} = 0 \quad (1)$$

The current I is equal to "-" change rate of charge Q in capacitor plates.

$$\text{So, as } \frac{dQ}{dt} < 0 \text{ and } I > 0 \text{ one gets } I(t) = -\frac{dQ(t)}{dt} \quad (*)$$

Then, by substituting relation (*) in eq.1 one gets

$$\frac{Q(t)}{C} + L \frac{d^2}{dt^2} Q(t) = 0 \rightarrow \frac{d^2}{dt^2} Q(t) + \frac{1}{LC} Q(t) = 0 \quad (2)$$

By noting $\omega_0^2 = \frac{1}{LC}$ -i.e.- $\omega_0 = \sqrt{\frac{1}{LC}}$, the eq.(2) takes the form $\frac{d^2}{dt^2} Q(t) + \omega_0^2 Q(t) = 0$ (3)

This is the equation of SHO and its solution has the form $Q(t) = Q_0 \sin(\omega_0 t + \varphi)$ (4)

At t = 0, Q = Q₀ that fixes $\varphi = \pi/2$. So, $Q(t) = Q_0 \sin(\omega_0 t + \pi/2) = Q_0 \cos(\omega_0 t)$ (5)

Then $I(t) = -\frac{dQ(t)}{dt} = Q_0 \omega_0 \sin \omega_0 t = I_0 \sin \omega_0 t$. So with $I_0 = Q_0 \omega_0$ $I(t) = I_0 \sin \omega_0 t$ (6)

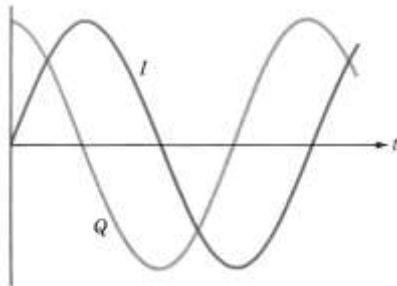


Fig.2

From expressions (1-6) comes out that: **"if there is some energy stored in a LC circuit, the circuit will generate a SHO with circular frequency**

$\omega_0 = \sqrt{\frac{1}{LC}}$ for the **current**, the **voltage** and the **charge in capacitor**.

Fig. 2 shows the variation of Q(t) and I(t) in time; the charge in capacitor and its voltage V_C = Q/C are **advanced** by π/2 versus the current in circuit. When Q_C and V_C are maximum the **current in circuit is zero** (and vice versa). At t = 0, **all the energy** is electric and stocked **inside the capacitor** :

$$U_{E-max} = \frac{Q_0^2}{2C} \quad (7)$$

For t > 0, a part of the energy is stocked as *electric energy inside the capacitor* $U_E = \frac{Q_0^2}{2C} \cos^2 \omega_0 t$ and

the other part as *magnetic energy inside the inductor* $U_B = \frac{1}{2} L I_0^2 \sin^2 \omega_0 t$; so the **total energy in circuit**

$$\text{is } U = \frac{Q_0^2}{2C} \cos^2(\omega_0 t) + \frac{L I_0^2}{2} \sin^2(\omega_0 t) \quad (8)$$

Figure 3 presents the evolution of each part of of energy with time. Note that their sum is **all time constant** (like at any SHO) and when one of them is maximum the other one is zero.

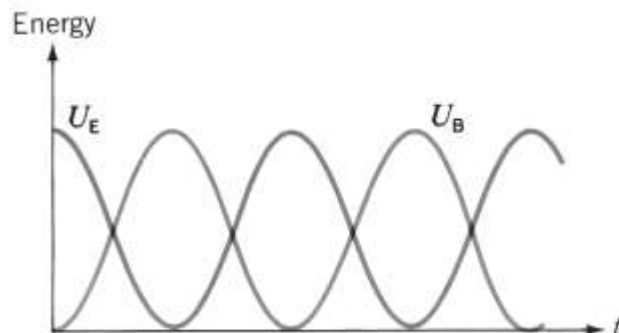


Fig 3

12.2 DAMPED OSCILLATIONS IN A CIRCUIT C, L, R

- In previous section we considered an *ideal inductor* with zero resistance and we got a result which is ideal; i.e. *SHO for Q, I and U in the circuit*. This means oscillations that follow to infinity time. Now, let's see the case of a real inductor; i.e. an inductor resistance R. In this case one has a circuit with C, L, R in series (fig.4). Assume that, initially, at t = 0s, the capacitor has its maximum charge Q₀.

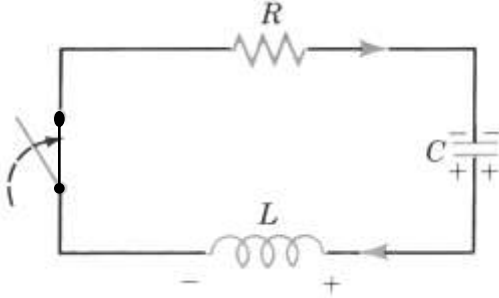


Fig.4

At this moment (t = 0) one turns the circuit " on ".
Let's apply the second rule of Kirchoff for a moment t > 0. We will get

$$\frac{Q(t)}{C} - L \frac{dI}{dt} - IR = 0 \quad (9)$$

By using the expression (*) for the current, we get

$$L \frac{d^2 Q(t)}{dt^2} + R \frac{dQ(t)}{dt} + \frac{Q(t)}{C} = 0 \quad (10)$$

This is the equation of a damped harmonic oscillation. One might remember the equation for damped

harmonic motions : $m \frac{d^2 x(t)}{dt^2} + b \frac{dx(t)}{dt} + kx(t) = 0$ where **b** is the damping coefficient.

By referring to DHO (NYC folder) , one finds out that the solution of (10) has the form

$$Q(t) = Q_0 * e^{-(R/2L)*t} \cos(\omega' t + \delta) \quad (11)$$

where the **damped circular frequency** is

$$\omega' = \sqrt{\omega_0^2 - \left(\frac{R}{2L}\right)^2} \quad (12)$$

The un-damped circular frequency for a C, L, R circuit corresponds to **R = 0** and is $\omega_0 = \frac{1}{\sqrt{LC}}$ (13)

- The evolution of electric parameters (**Q, I, U**) in circuit depends on the relative values of **R, L and C**.

- There are under damped oscillations if **R < 2ω₀L**. The amplitude of oscillations for (**Q, I, U**) decays exponentially. **Example (Fig.5a):** $Q(t) = Q_0 * e^{-t/\tau}$ where $\tau = 2L/R$ (14)
- There are critically damped oscillations if **R = 2ω₀L**. **Actually, in this case there are no oscillations in circuit. All electric variables just fall to zero the fastest way (Fig.5b-down).**
- There are over damped oscillations if **R > 2ω₀L**. **Even in this case there are no oscillations in circuit. All electric variables just fall to zero with time, but slowly (Fig.5b-up).**


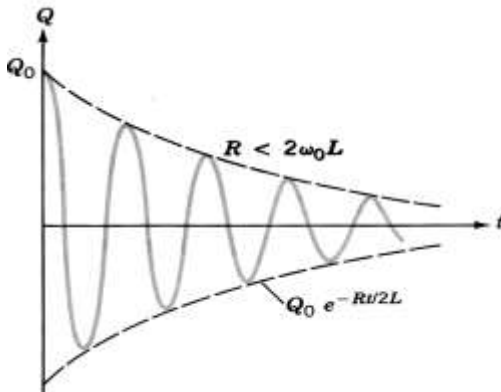


Fig.5 (a)

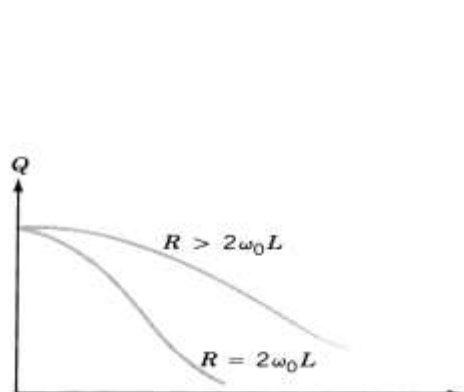

(b)